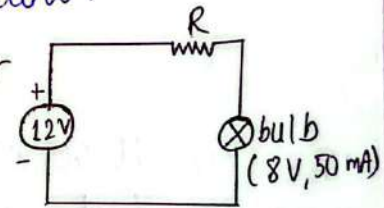


Qno.1

- a) Resistance of a lamp (R) = $28 \frac{1}{8} \Omega = \frac{225}{8} \Omega$
 Total resistances in series = $\frac{225}{8} \times 8 = 225 \Omega$
 $\therefore$ Current through the bulbs (I) = $\frac{120}{225} = 0.533 A$
- b) Power in each bulb = $I^2 R = \left(\frac{8}{15}\right)^2 \times \frac{225}{8} = 10 W$
- c) voltage drop across each bulb = $I \cdot R = \frac{8}{15} \times \frac{225}{8} = 15 V$
- d) As all the bulbs are in series, if one bulb burns out the circuit will be open and none of the bulb would glow.

Qno.2 The voltage divider circuit for the given condition is as shown below.

As the bulb requires 8V, the resistor should have a voltage drop
 $= (12 - 8) V = 4 V$



Also as the resistor are in series with the bulb same current flow in both resistor and bulb i.e. 50mA.

$$\therefore \text{The resistance, } R = \frac{4 V}{50 \text{ mA}} = 80 \Omega$$

$$\text{Also the power in the resistance} = 4 V \times 50 \text{ mA} = 0.2 W$$

$\therefore$ From the available resistors, the minimum wattage rating of the resistor R will be 0.25 W.

Qno.3

(a) The current through each 60 W lamp = $\frac{60 \text{ W}}{120 \text{ V}} = 0.5 \text{ A}$

The current through 400 W toaster = $\frac{400 \text{ W}}{120 \text{ V}} = 3.33 \text{ A}$

The current through 360 W TV = $\frac{360 \text{ W}}{120 \text{ V}} = 3 \text{ A}$

(b) The total current drawn from the 120 V source
 $= 10 \times 0.5 + 3.33 + 3$
 $= 11.33 \text{ A}$

The circuit breaker is rated as 20 A (i.e. it will open when the current exceeds 20 A). For the given load the maximum current = $11.33 \text{ A} < 20 \text{ A}$ i.e. less than the circuit breaker rating so the circuit breaker will not open.

(c) The total resistance of the network = $\frac{\text{Total Voltage}}{\text{Total current}}$
 $= \frac{120}{11.33} = 10.588 \Omega$

d) The circuit connection & the circuit breaker rating specifies that, the maximum power that can be supplied by the source = $120 \text{ V} \times 20 \text{ A} = 2400 \text{ W}$

The total power of the load = $60 \text{ W} \times 10 + 400 \text{ W} + 360 \text{ W}$
 $= 1360 \text{ W}$

$\therefore$ other loads upto $2400 - 1360 = 1040 \text{ W}$ can also be connected to the source.

Qno. 4

a) The open circuit voltage $V_L = \frac{4.7 \times 10^3 \times 9}{2.2 \times 10^3 + 4.7 \times 10^3} = 6.13 \text{ V}$




(b) If $2.2 \text{ k}\Omega$ is short circuited, the voltage sources becomes parallel to $4.7 \text{ k}\Omega$ resistance,

$$\therefore V_L = 9 \text{ V}$$

(c) If $4.7 \text{ k}\Omega$ resistor is open circuited, there will be no current in the circuit i.e. no voltage drop in resistors, $\therefore V_L = 9 \text{ V}$

Qno. 5

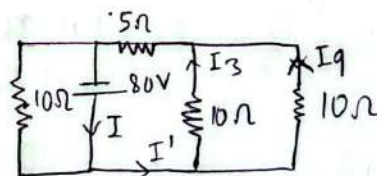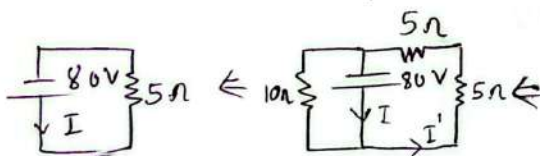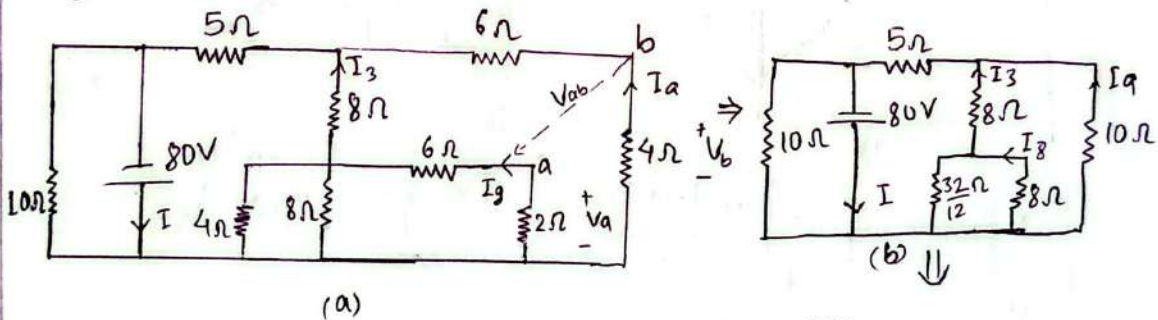a) The current I can be determined by finding the total resistance in parallel to the voltage source. Thus to find the equivalent resistance the circuit is reduced as under:



$\therefore$ Equivalent resistance across the source $= 5 \Omega$

$$\therefore \text{The current } I = \frac{80}{5} = 16 \text{ A}$$

(b) As per the figure (d) the current $I' = \frac{16 \times 10}{10 + 10} = 8 \text{ A}$

$$\therefore \text{The current } I_3 \text{ as shown in figure (c)} = \frac{10 \cdot I'}{10 + 10} = \frac{10 \times 8}{20} = 4 \text{ A}$$

$$\text{Hence, current } I_9 = \frac{10 \times 8}{20} = 4 \text{ A}$$

$$[\text{Or, } I_9 = I' - I_3 = 8 - 4 = 4 \text{ A}]$$

(c) As per the figure (b) the current I_3 divides in two lower branch and current of one lower branch is I_8 .

$$\therefore I_8 = \frac{\frac{32}{12} \times I_3}{\frac{32}{12} + 8} = \frac{\frac{32}{12} \times 4}{\frac{32}{12} + 8} = 1A$$


(d) The voltage V_{ab} is the difference of voltage V_a & V_b as in figure (a).

$$V_a = 2\Omega \times (-I_8) = -2V$$

$$V_b = 4\Omega \times (-I_9) = 4 \times -4 = -16V$$

$$\therefore V_{ab} = -2 - (-16V) = 14V$$

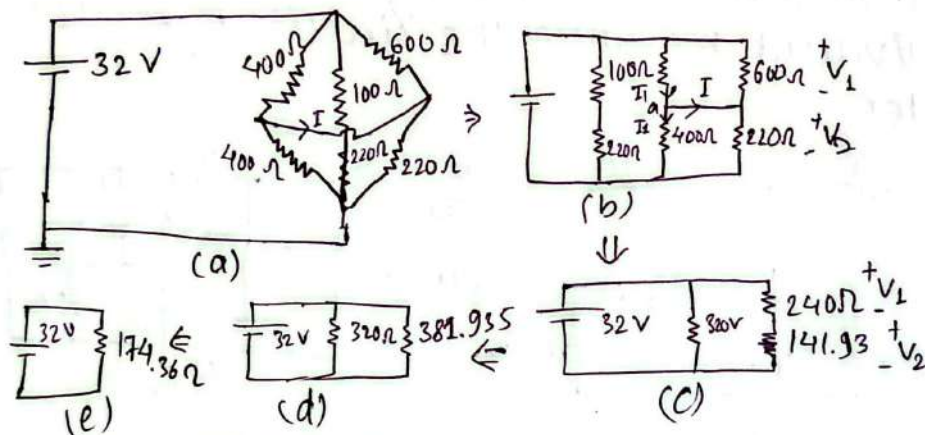6a. The equivalent resistance is found as shown in figures



(b) $V_a = V_2 = \frac{32 \times 141.93}{240 + 141.93} = 11.89V$

(c) $V_1 = 32 - 11.89 = 20.108V$

(d) $V_2 = 11.89V$

(e) As per fig (b),

$$I_1 = \frac{20.108}{400} = 0.05027A$$

$$I_2 = 0.029725A$$


$$I = I_1 - I_2 = 0.02054A$$

The direction will be as marked in fig (b)

(7a) The circuit with voltage source becomes as shown below

Here, $V_s = 2A \times 6.8\Omega = 13.6V$

$R_i = 6.8\Omega$

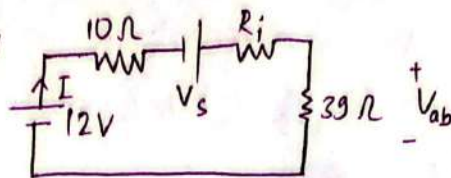


(b) Here,

The magnitude of current $(I) = \frac{(12 + 13.6)V}{(10 + 6.8 + 39)\Omega} = 0.45878A$


the direction would current coming out from the +ve terminal of the 12V source as shown in figure above

(c) The polarity of the voltage V_{ab} is as marked in above figure, The magnitude of $V_{ab} = 39\Omega \times 0.45878 = 17.89V$

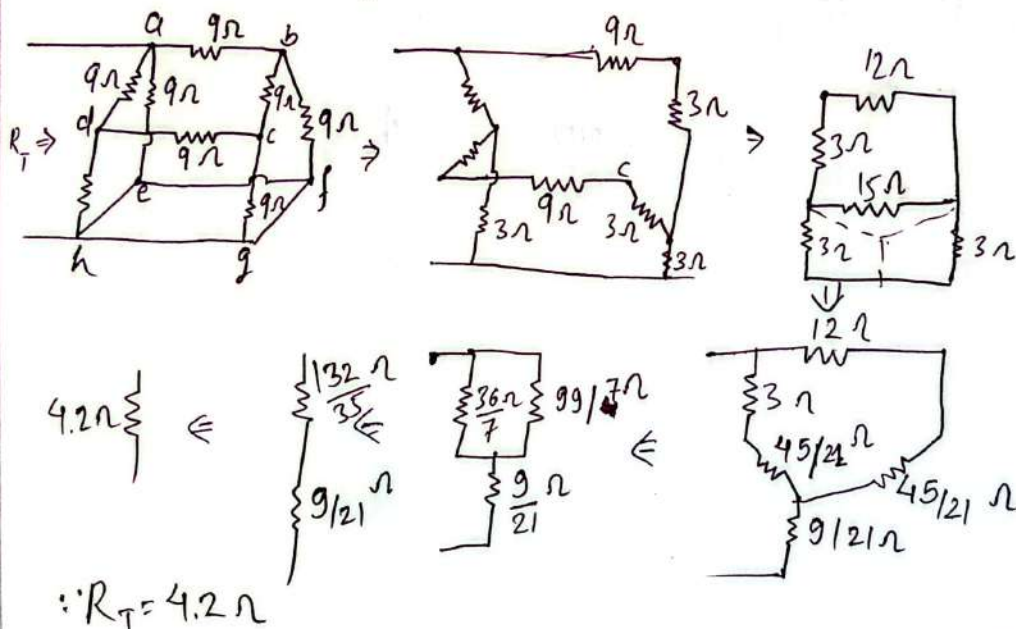
(8) The total resistance of the network is determined as shown in figure below:



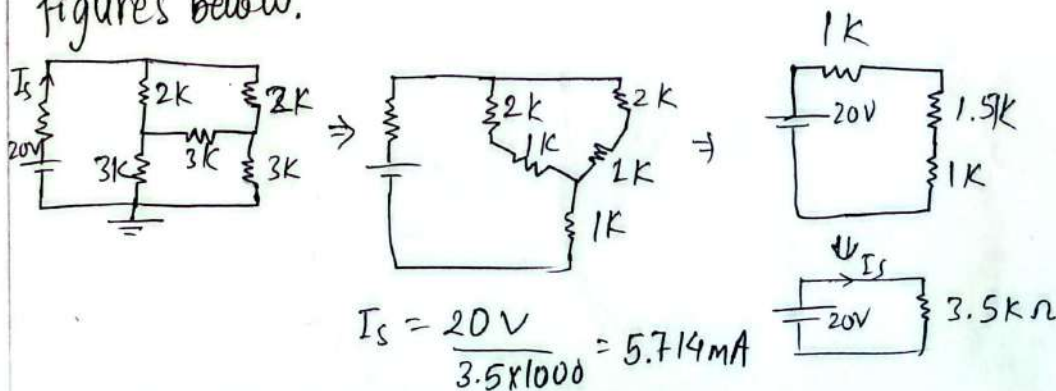(9) To get the current I_s , the equivalent resistance across the voltage source (20V) is determined as shown in figures below.



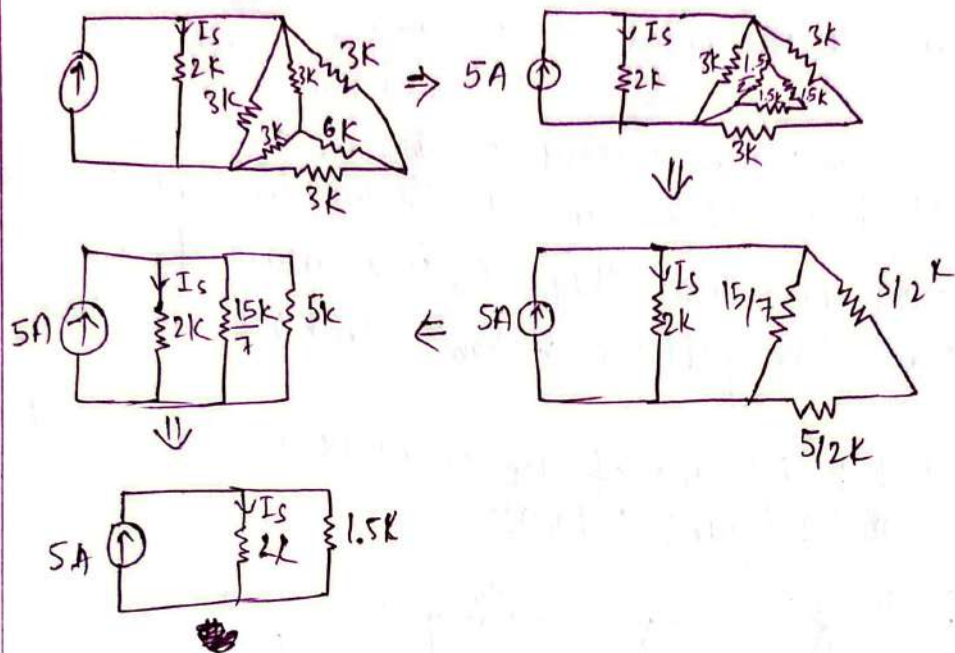10) To determine the current, the equivalent resistance for the Δ & Y network is ~~equa~~ evaluated as shown below & I_s is determined using current divider rule.



$$\therefore I_s = \frac{5 \times 1.5 \times 1000}{2000 + 1500} = 2.14 A$$