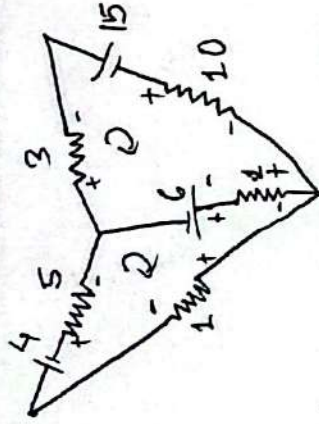


1) a)



For Mesh 1, $(-7)I_1 + (1)I_2 = -2$ — (i)


For Mesh 2, $1I_1 + (-14)I_2 = 21$ — (ii)

From (i) & (ii),

$$I_1 = 0.07 \text{ A}$$

$$I_2 = -1.5 \text{ A}$$

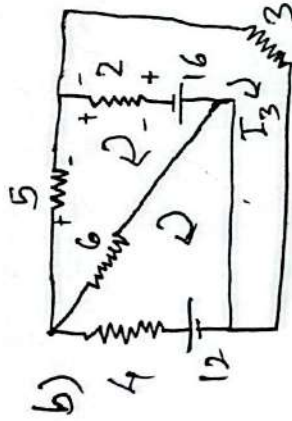$\therefore$ Current through 5Ω resistor is 0.07 A right.



For mesh 1, $-10 I_1 + 6 I_2 + 0(I_3) = -12$ — (1)

For mesh 2, $6 I_1 + (-13) I_2 + 2 I_3 = -16$ — (2)

For mesh 3, $0 I_1 + 2 I_2 + 5 I_3 = 16$ — (3)

solving (1), (2) & (3),


$$I_1 = 2.94 \text{ A}$$

$$I_2 = 2.9 \text{ A}$$

$$I_3 = 2.04 \text{ A}$$

$\therefore$ Current through 5Ω resistor is 2.9 A right.

2 (a)

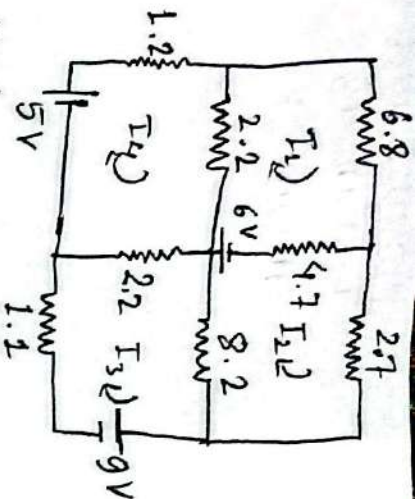

For Mesh 1, $-13.7I_1 + 4.7I_2 + 0I_3 + 2.2I_4 = -6$ — (1)

For Mesh 2, $4.7I_1 + (-15.6)I_2 + 8.2I_3 + 0I_4 = 6$ — (2)

For Mesh 3, $0I_1 + 8.2I_2 + (-31.3)I_3 + 22I_4 = 9$ — (3)

For Mesh 4, $2.2I_1 + 0I_2 + 22I_3 + (-25.4)I_4 = -5$ — (4)

On solving,


$$I_1 = -0.032 \text{ mA}$$

$$I_2 = -0.883 \text{ mA}$$

$$I_3 = -0.968 \text{ mA}$$

$$I_4 = -0.639 \text{ mA}$$

(b)

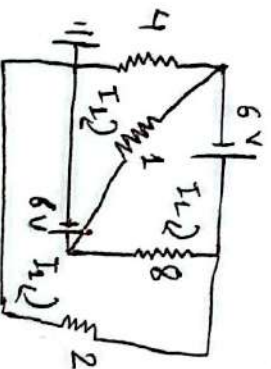

For Mesh 1, $-5I_1 + 1I_2 + 0I_3 = 6$ — (1)

For Mesh 2, $1I_1 - 9I_2 + 8I_3 = -6$ — (2)

For Mesh 3, $0I_1 + 8I_2 - 10I_3 = -6$ — (3)

On solving,


$$I_1 = -3.8 \text{ A}$$

$$I_2 = -4.2 \text{ A}$$

$$I_3 = 0.2 \text{ A}$$

(3)

a)

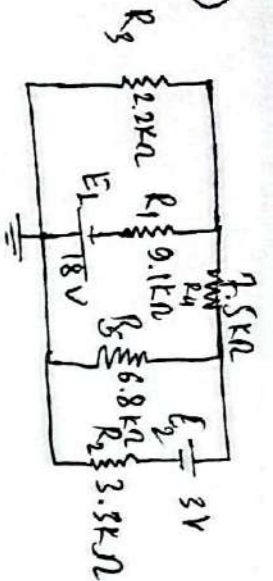

For mesh 1,

$$-11.3 I_1 + 9.1 I_2 + 0 I_3 = -18 \quad (1)$$

For mesh 2,

$$9.1 (I_1) + (-23.4) I_2 + 6.8 I_3 = 18 \quad (2)$$

For mesh 3,

$$0 I_1 + 6.8 I_2 - 10.1 I_3 = 3 \quad (3)$$

Solving these,

$$I_1 = 1.2 \text{ mA}$$

$$I_2 = -0.48 \text{ mA}$$

$$I_3 = -0.62 \text{ mA}$$

$$\therefore 2.2 \text{ k}\Omega \rightarrow 1.2 \text{ mA up}$$


$$3.3 \text{ k}\Omega \rightarrow 0.62 \text{ mA up}$$

$$7.5 \text{ k}\Omega \rightarrow 0.48 \text{ mA left}$$

$$9.1 \text{ k}\Omega \rightarrow 1.68 \text{ mA down}$$

$$6.8 \text{ k}\Omega \rightarrow 0.14 \text{ mA down}$$

4(a)

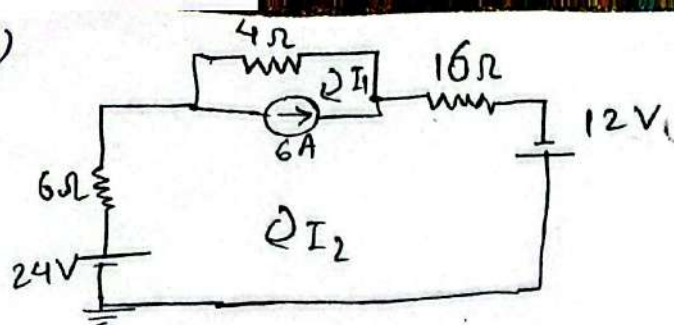

$$I_2 - I_1 = 6$$

$$-I_1 + 2I_2 = 6 \quad \text{--- (1)}$$

using supermesh,

$$-4I_1 - 16I_2 = -24 - 12$$


$$-4I_1 - 16I_2 = -36 \quad \text{--- (2)}$$

From (1) & (2),

$$\therefore I_1 = -3A$$

$$I_2 = 3A$$

(b)

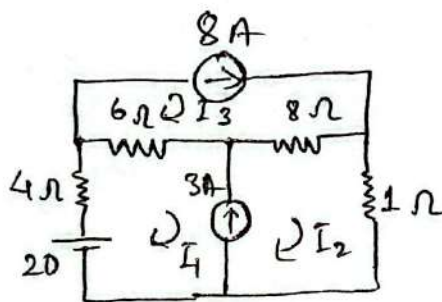

$$I_3 = 8A$$

using supermesh,

$$-10I_1 + 6I_3 - 9I_2 + 8I_3 = -20$$

$$\text{or, } -10I_1 - 9I_2 = -132 \quad \text{--- (1)}$$

Now


$$I_2 - I_1 = 3$$

$$-I_1 + I_2 = 3 \quad \text{--- (2)}$$

Solving (1) & (2), we get

$$I_1 = 5.52A$$

$$I_2 = 8.52A$$

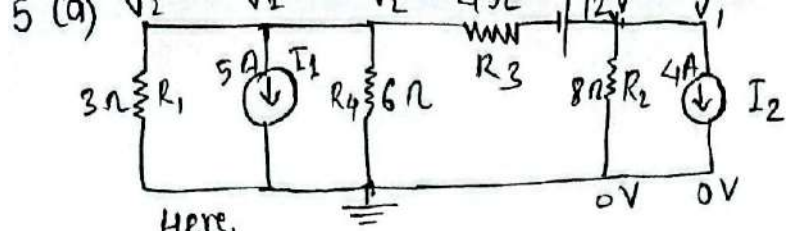

Here,

$$V_1 - V_2 = 12$$

$$-V + V_1 + 0V_2 = 12 \quad \text{--- (1)}$$

using node analysis,

$$I = \frac{V_1}{8} + 4 = \frac{-V_2}{6} - \frac{V_2}{3} - 5 = \frac{V_2 - V}{4}$$

$$I = \frac{V_1}{8} + 4 = \frac{-V_2}{2} - 5 = \frac{V_2 - V}{4}$$

$$\text{or, } \frac{1}{8} V_1 + \frac{1}{2} V_2 = -9$$

$$\text{or, } 0V + \frac{1}{8} V_1 + \frac{1}{2} V_2 = -9 \quad \text{--- (2)}$$

And,


$$\frac{1}{4} V + \frac{1}{8} V_1 - \frac{1}{4} V_2 = -4 \quad \text{--- (3)}$$

After solving (1), (2) & (3),

$$V = -24.57 \text{ V}$$

$$V_1 = -12.57 \text{ V}$$

$$V_2 = -14.85 \text{ V}$$

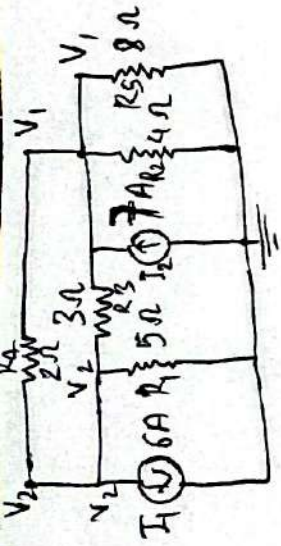

Here,

$$6 = -\frac{V_2}{5} + 7 - \frac{V_1}{4} - \frac{V_1}{8}$$

$$\text{or, } \frac{3}{8} V_1 + \frac{1}{5} V_2 = 1 \quad \text{--- (1)}$$

And,

$$7 - \frac{V_1}{4} - V_1 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_2}{2}$$

$$\text{or, } 7 = \frac{29}{24} V_1 - \frac{5}{6} V_2 \quad \text{--- (2)}$$

Solving these,

$$V_1 = 4.03 \text{ V}$$

$$V_2 = -2.55 \text{ V}$$

$$2\Omega \rightarrow 6.58 \text{ V}$$


$$3\Omega \rightarrow 6.58 \text{ V}$$

$$4\Omega \rightarrow 4.03 \text{ V}$$

$$5\Omega \rightarrow -2.55 \text{ V}$$

$$8\Omega \rightarrow 4.03 \text{ V}$$

6(b)

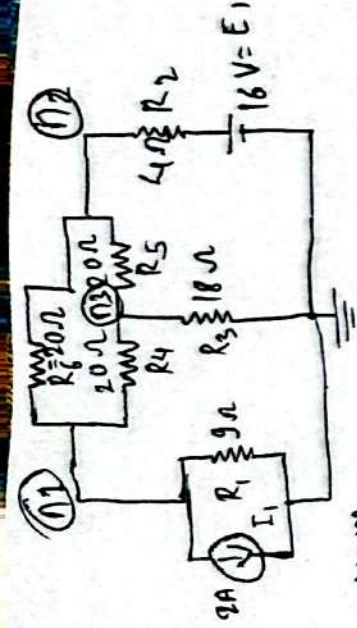

Here,

$$I = \frac{V_2 - V_1}{20} + \frac{V_2 - V_3}{20} = \frac{V_3}{18} + 2 + \frac{V_1}{9} = \frac{16 - V_2}{4}$$

$$\text{or, } -\frac{V_1}{20} + \frac{V_2}{10} - \frac{V_3}{20} = \frac{V_1}{9} + \frac{V_3}{18} + 2 = 4 - \frac{V_2}{4}$$

$$\left(-\frac{1}{20}\right)V_1 + \left(\frac{7}{20}\right)V_2 - \left(\frac{1}{20}\right)V_3 = 4 \quad \text{--- (1)}$$

$$\left(\frac{1}{9}\right)V_1 + \left(\frac{1}{4}\right)V_2 + \left(\frac{2}{18}\right)V_3 = 2 \quad \text{--- (2)}$$

similarly,

$$\frac{V_2 - V_3}{20} = \frac{V_3}{18} + \frac{V_3 - V_1}{20}$$


$$\text{or, } \frac{1}{20}V_1 + \frac{1}{20}V_2 - \frac{7}{45}V_3 = 0 \quad \text{--- (3)}$$

solving these we get,

$$V_{\text{node 1}} = -6.64 \text{ V}$$

$$V_{\text{node 2}} = 10.66 \text{ V}$$

$$V_{\text{node 3}} = 1.3 \text{ V}$$

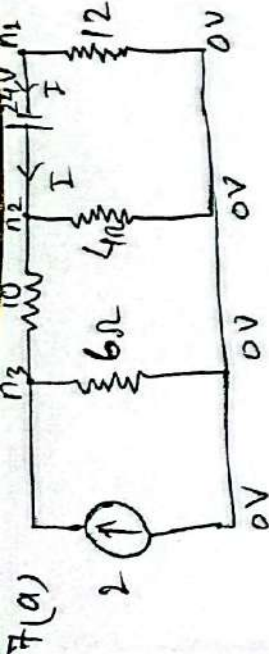

Here,

$$\frac{V_2 - V_3}{10} + \frac{V_2}{4} = \frac{-V_1}{12} = \frac{V_2}{4} + \frac{V_3}{6} - 2$$

$$\text{or, } \frac{V_2 - V_3}{10} + \frac{V_2}{4} = \frac{-V_1}{12} = \frac{V_2 + \frac{V_3}{6} - 2}{1}$$

$$\left(\frac{1}{12}\right)V_1 + \frac{7}{20}V_2 - \frac{1}{10}V_3 = 0 \quad \text{--- (1)}$$

$$0V_1 + \frac{1}{10}V_2 - \frac{4}{15}V_3 = -2 \quad \text{--- (2)}$$

Also,

$$V_2 - V_1 = 24$$

$$-1V_1 + V_2 + 0V_3 = 24 \quad \text{--- (3)}$$


solving these we get,

$$V_{\text{node } 1} = -17.05 \text{ V}$$

$$V_{\text{node } 2} = 6.95 \text{ V}$$

$$V_{\text{node } 3} = 10.1 \text{ V}$$

7 (b)

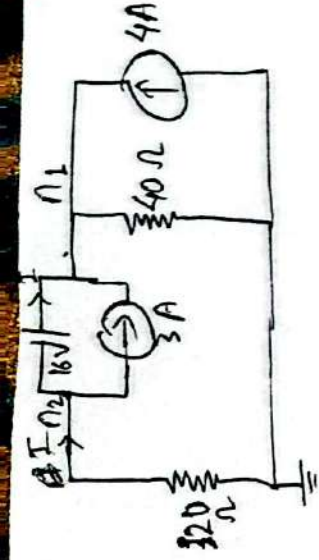

Here,

$$I + I_3 = \frac{V_1}{40}$$

$$I = \frac{V_1}{40} - 7 \quad \text{--- (1)}$$

And $-\frac{V_2}{20} = I + 3$

$$\text{or, } I = -\frac{V_2}{20} - 3 \quad \text{--- (2)}$$

From (1) & (2)

$$\frac{V_1}{40} - 7 = -\frac{V_2}{20} - 3$$

$$\text{or, } \frac{1}{40} V_1 + \frac{1}{20} V_2 = 4 \quad \text{--- (3)}$$


$$\underline{\text{By,}} \quad 1V_1 + (-2)V_2 = 16 \quad \text{--- (4)}$$

on solving (3) & (4), we get,

$$V_{\text{node 1}} = 64 \text{ V}$$

$$V_{\text{node 2}} = 48 \text{ V}$$

6(a)

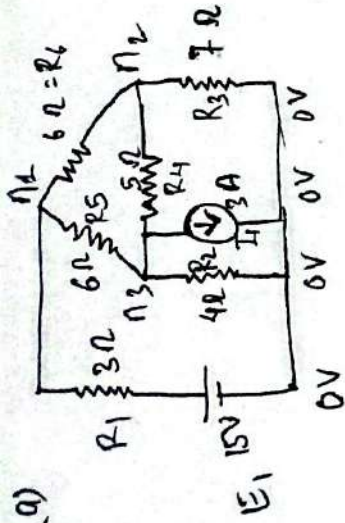

using node analysis,

$$\frac{V_1 - V_3 + V_1 - V_2}{6} = \frac{V_3}{4} + 3 + \frac{V_2}{7} = \frac{15 - V_1}{3}$$

$$\text{or, } \frac{V_1 - V_2}{3} - \frac{V_3}{6} = \frac{V_2}{7} + \frac{V_3}{4} + 3 = 5 - \frac{V_1}{3}$$

$$\left(\frac{2}{3}\right)V_1 + \left(-\frac{1}{6}\right)V_2 + \left(-\frac{1}{6}\right)V_3 = 5 \quad \text{--- (1)}$$

$$\left(\frac{1}{3}\right)V_1 + \left(\frac{1}{7}\right)V_2 + \left(\frac{1}{7}\right)V_3 = 2 \quad \text{--- (2)}$$

Similarly,

$$\frac{V_1 - V_2}{6} = \frac{V_2}{7} + \frac{V_2 - V_3}{5}$$

$$\frac{V_1 - V_2}{6} - \frac{V_2}{7} - \frac{V_1}{5} + \frac{V_3}{5} = 0$$

$$\frac{1}{6}V_1 + \left(-\frac{107}{210}\right)V_2 + \left(\frac{1}{5}\right)V_3 = 0 \quad \text{--- (3)}$$

solving these we get,

$$V_{\text{node1}} = 6.94 \text{ V}$$

$$V_{\text{node2}} = 1 \text{ V}$$

$$V_{\text{node3}} = -3.21 \text{ V}$$